

PART – B

(5 x 13 = 65 Marks)

Q.No.	Questions	Marks	KL	CO
11. a)	i. Find complement of the following Boolean expression. $Y = xyz' + x'yz + z(xy+w)$	5	K3	CO1
	ii. What are universal gates? Implement the following expression using only NOR gate and using only NAND gate. $Y = (B+C)(B+D')(A+C)$ (OR)	4+4	K1	CO1
b)	Simplify the given boolean function in Product-of-Sum (POS) form using Kmap and draw the logic diagram using Only NOR gates $F(A,B,C,D) = \sum_m (0,1,4,7,8,10,12,15) + d(2,6,11,14)$.	13	K3	CO1
12. a)	Design a full adder with neat sketch. Implement full adder with two half adders and an OR gate. (OR)	13	K2	CO2
b)	i. Implement the following functions using 4X1 multiplexers. $F(W,X,Y,Z) = \sum_m (0,1,3,4,8,9,15)$.	9	K3	CO2
	ii. Implement a 4 bit even parity checker.	4	K2	CO2
13. a)	Using D Flip-Flop, design a synchronous counter that counts the sequence $000 \rightarrow 001 \rightarrow 010 \rightarrow 011 \rightarrow 100 \rightarrow 101 \rightarrow 110 \rightarrow 111 \rightarrow 000$. (OR)	13	K3	CO3
b)	i. Realize D flip-flop using SR Flip-Flop.	5	K1	CO3
	ii. Explain the working philosophy of a 3-bit universal shift register with a neat sketch.	8	K2	CO3
14. a)	An asynchronous sequential circuit is described by the following excitation and output function, $Y = X_1X_2 + (X_1 + X_2)Y$ and $Z = Y$.		K3	CO4
	i. Draw the logic diagram of the circuit.	5		
	ii. Derive a transition table, flow table and output map and describe the behavior of the circuit. (OR)	8		
b)	Discuss the various types of hazard. How to design a hazard free circuits, explain with example?	13	K1	CO4

15. a) Why it is necessary to use a ROM in personal computers? 13 K2 CO5
Explain various types of ROM in detail.

(OR)

- b) Explain in detail about the Programmable Logic Array (PLA), Programmable Array Logic (PAL) and Field Programmable Gate Arrays (FPGA). 13 K2 CO5

PART – C

(1 x 15 = 15 Marks)

Q.No.	Questions	Marks	KL	CO
16. a)	Design a BCD to Excess-3-code converter using minimum number of NAND gates.	15	K3	CO2
(OR)				
b)	Design a counter using JK flip-flops with a following binary sequence: 1, 2, 5, 7 and repeat.	15	K3	CO3