

Reg.No.:



VIVEKANANDHA COLLEGE OF ENGINEERING FOR WOMEN
[AUTONOMOUS INSTITUTION AFFILIATED TO ANNA UNIVERSITY, CHENNAI]
Elayampalayam – 637 205, Tiruchengode, Namakkal Dt., Tamil Nadu.



Question Paper Code: 7012

B.E. / B.Tech. DEGREE SUPPLEMENTARY EXAMINATIONS – FEB. / MAR. 2020

Third Semester

Computer Science and Engineering

U15EC305 – DIGITAL LOGIC DESIGN

(Common to Information Technology)

(Regulation 2015)

Time : Three Hours

Maximum : 100 Marks

Answer ALL the questions

PART – A

(10 x 2 = 20 Marks)

1. State De Morgan's theorem.
2. Convert the hexadecimal number ABCD to binary.
3. State the limitations of karnaugh map.
4. Convert the given expression in canonical SOP form $Y = AC + AB + BC$.
5. Write the function of magnitude comparator.
6. Compare the function of Encoder and Decoder.
7. Write the differences between synchronous and asynchronous counters.
8. Derive the flip-flop excitation table for D flip-flop.
9. Differentiate between Moore's and mealy's model.
10. When does race condition occur?


PART – B

(5 x 13 = 65 Marks)

11. a) i. State and prove any 3 laws of Boolean Algebra. (6)
ii. Apply Boolean algebra to simplify the expression and realize using only NAND gates. $Y = (AB + C')D + EF$. (7)
- (OR)

 - b) i. Convert the hexadecimal number $B5_{(16)}$ to decimal and octal.(4)
 ii. Reduce the following Boolean expressions to the indicated number of literals:
- $A^*C^* + ABC + AC^*$ to three literals (2)
 - $(x^*y^*+z)^* + z + xy + wz$ to three literals (2)
 - $A^*B(D^*+C^*D) + B(A+A^*CD)$ to one literal (3)
 - $(A^*+C)(A^*+C^*)(A+B+C^*D)$ to four literals (2)
12. a) Find all the prime implicants for the following Boolean function (using K-Map) and determine which are essential and implement with NAND gates.

$$F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14).$$
 (OR)
- b) Minimize $f(A, B, C, D) = (0, 1, 2, 3, 5, 7, 8, 10, 12, 13, 15)$ using Quine-McCluskey method.
13. a) i. Design a full subtractor using 1-to-8 Demultiplexer. (6)
 ii. Design a 4-bit Magnitude Comparator with logic diagram. (7)
 (OR)
- b) Implement the following function using PAL.
- $W(A, B, C, D) = \sum m(2, 12, 13)$ (4)
 - $X(A, B, C, D) = \sum m(7, 8, 9, 10, 11, 12, 13, 14, 15)$ (3)
 - $Y(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$ (3)
 - $Z(A, B, C, D) = \sum m(1, 2, 8, 12, 13)$ (3)
14. a) i. With relevant diagram explain the working of master-slave JK flip flop. (5)
 ii. Evaluate the following state diagram and tabulate the reduced state table. Consider the input sequence 01010110100 starting from the initial state a. (8)



(OR)

- b) Design a mod-5 up/down counter using JK-FF. Draw the realization diagram.
15. a) Illustrate how to avoid races, cycles in asynchronous sequential circuits with suitable examples.
- (OR)
- b) i. Explain the types of hazards in sequential circuits with examples. (7)
ii. Write a technical note on "Design of asynchronous sequential circuits". (6)

PART – C

(1 x 15 = 15Marks)

16. a) Draw state transition diagram of sequence detector circuit that detects 1101 from input data stream using both Mealy and Moore model.
- (OR)
- b) i. Design a gated latch circuit which have two inputs G and D and one output Q. The output Q retains its previous state value if the input $G = 0$ regardless of the input D. The output Q will follow the input D if the gated Latch input $G = 1$. (7)
ii. Simplify the function F using K-map where $F = \pi(0, 1, 4, 5, 13)$ (8)

