

Reg.No.:



VIVEKANANDHA COLLEGE OF ENGINEERING FOR WOMEN
[AUTONOMOUS INSTITUTION AFFILIATED TO ANNA UNIVERSITY, CHENNAI]
Elayampalayam – 637 205, Tiruchengode, Namakkal Dt., Tamil Nadu.



Question Paper Code: 8001

B.E. / B.Tech. DEGREE SUPPLEMENTARY EXAMINATIONS – FEB. / MAR. 2020

Third Semester

Computer Science and Engineering

U15EE309 - INTRODUCTION TO ELECTRICAL AND ELECTRONICS CIRCUITS

(Common to Information Technology)

(Regulation 2015)

Time : Three Hours


Maximum : 100 Marks

Answer ALL the questions

PART – A

(10 x 2 = 20 Marks)

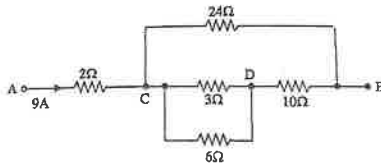1. Determine the effective resistance between terminals A & B in the given circuit.




- State Thevenin's theorem.
- Write the expression for transient current for series RL and RC circuits.
- Define Q-factor.
- Demonstrate the Mass-action law.
- Compare Avalanche breakdown and Zener breakdown.
- Differ FET with MOSFET.
- Write a short note about n channel JFET.
- List some application of DIAC.
- What is meant by Tunnel diode?

PART - B


(5 x 13 = 65 Marks)

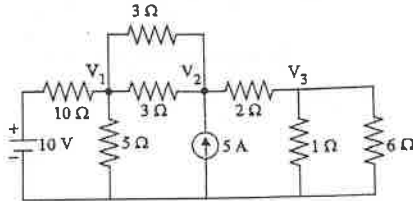11. a) Determine the voltages at each node for the given circuit.




(OR)

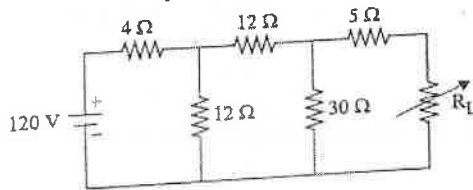- b) Find the load resistance for maximum power across it as shown in fig. What is the maximum power?



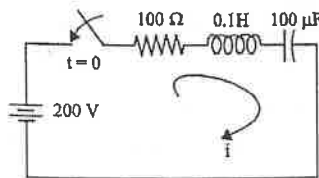12. a) A series RLC circuit with $R = 100 \Omega$, $L = 0.1 \text{ H}$ and $C = 100 \mu\text{F}$ has a DC voltage of 200 V applied to it at $t = 0$ through a switch. Find the expression for the transient current. Assume initially relaxed circuit conditions.



(OR)

- b) Construct an expression for the transient current of RC circuit with DC excitation.
13. a) Explain the V-I characteristics and Energy band structure of P-N Junction diode with a neat sketch.

(OR)

- b) Elaborate the concept of Zener diode and its characteristics with neat sketches.
14. a) Construct the working principle of MOSFET with a neat sketch.
(OR)
- b) Build the input and output characteristics of a transistor in CC configuration with a neat sketch.
15. a) Explain in detail about DIAC and TRIAC with neat sketches.
(OR)
- b) Explain in detail about PIN diode with a neat sketch.

PART – C

(1 x 15 = 15 Marks)

16. a) Construct an expression for Star to Delta and Delta to Star in DC circuits.
(OR)
- b) Elaborate the two transistor model of SCR with a neat sketch.
-

