

Reg.No.:									
----------	--	--	--	--	--	--	--	--	--



VIVEKANANDHA COLLEGE OF ENGINEERING FOR WOMEN
 [AUTONOMOUS INSTITUTION AFFILIATED TO ANNA UNIVERSITY, CHENNAI]
 Elayampalayam – 637 205, Tiruchengode, Namakkal Dt., Tamil Nadu.

Question Paper Code: 8033

B.E. / B.Tech. DEGREE END-SEMESTER EXAMINATIONS – AUG. / SEP. 2023

Second Semester

Electrical and Electronics Engineering

U19EE202 – ELECTRIC CIRCUIT THEORY

(Regulation 2019)

Time: Three Hours

Maximum: 100 Marks


Answer ALL the questions

Knowledge Levels (KL)	K1 – Remembering	K3 – Applying	K5 - Evaluating
	K2 – Understanding	K4 – Analyzing	K6 - Creating


PART – A

(10 x 2 = 20 Marks)

Q.No.	Questions	Marks	KL	CO
1.	Two resistors 4Ω and 6Ω are connected in parallel. If the total current is 20A, find the current across each resistor.	2	K1	CO1
2.	Determine the power factor of a RLC series circuit with $R=5\Omega$, $X_L=8\Omega$ and $X_C=12\Omega$.	2	K2	CO1
3.	In the figure determine the equivalent resistance by using star delta transformation.	2	K1	CO2

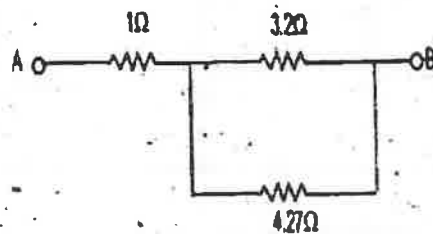

4.	Find the value of R_L for the maximum power transfer.	2	K1	CO2
----	---	---	----	-----

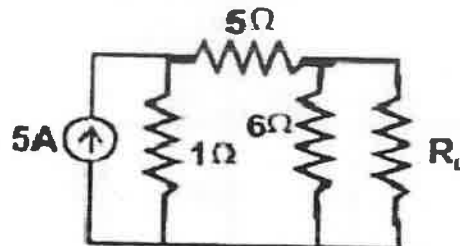


- | | | | | |
|---|---|---|----|-----|
| 5. | An RLC circuit consists of a resistance of 1000 W, an inductance of 100 mH and a capacitance of 10 μF. What is the Q factor of the circuit? | 2 | K1 | CO3 |
| 6. | Two coupled coils have a self inductances 37.5 mH and 193 mH, with the mutual inductance of 63.75 mH. Find the co efficient of coupling. | 2 | K1 | CO3 |
| 7. | Three loads, each of resistance 30Ω, are connected in star to a 415 V, 3-phase supply. Determine the phase current and the line current. | 2 | K1 | CO4 |
| 8. | Two wattmeters connected to a 3-phase motor indicate the total power input to be 12 kW. The power factor is 0.6. Determine the readings of each wattmeter. | 2 | K1 | CO4 |
| 9. | Construct a circuit that realizes the following Z parameters. | 2 | K2 | CO5 |
| $Z = \begin{bmatrix} 12 & 4 \\ 4 & 8 \end{bmatrix}$ | | | | |
| 10. | An alternating current $i = 414 \sin(2\pi \times 50 \times t)$ A is passed through a series circuit of a resistance of 100 ohm and an inductance of 0.31831 H. Find the expression for the instantaneous values of voltage across the resistance. | 2 | K2 | CO5 |

PART – B


(5 x 13 = 65 Marks)

- | | | | | |
|--------|---|-------|----|-----|
| Q.No. | Questions | Marks | KL | CO |
| 11. a) | Use nodal analysis to determine i_0 and V_R . | 13 | K2 | CO1 |

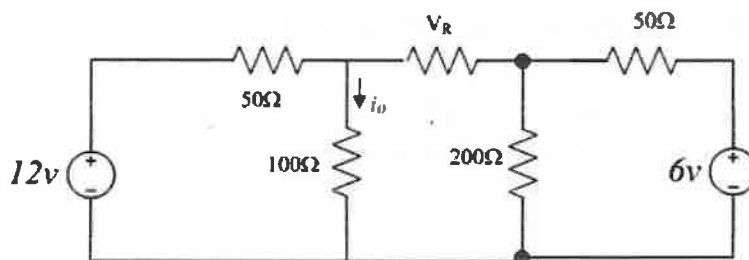


(OR)

- | | | | | |
|----|--|----|----|-----|
| b) | In the circuit shown in Figure determine the current I_x . | 13 | K2 | CO1 |
|----|--|----|----|-----|

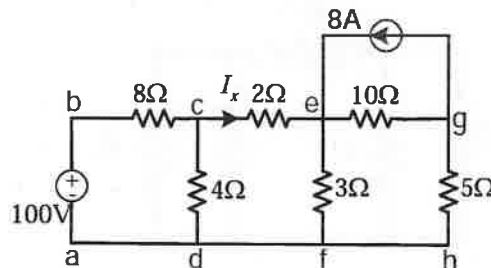

12. a) Find the current flowing through $20\ \Omega$ using the superposition theorem.


13 K1 CO2

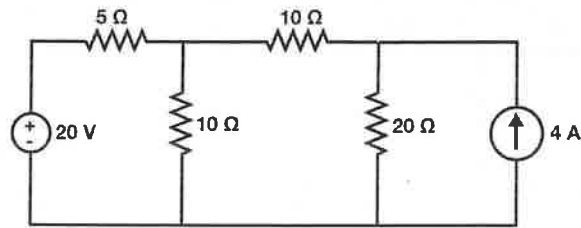

(OR)

- b) Find V_{TH} , R_{TH} and the load current I_L flowing through and load voltage across the load resistor in the circuit below using Thevenin's Theorem.

13 K1 CO2

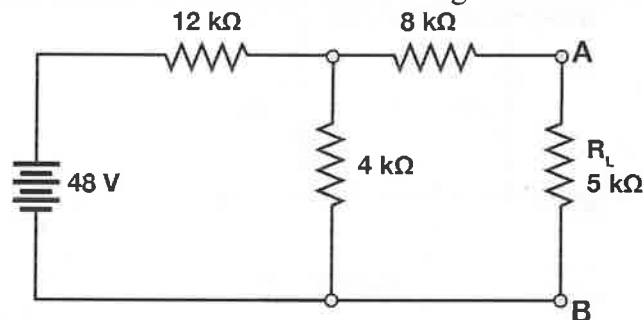

13. a) A series L-R-C circuit has a sinusoidal input voltage of maximum value 12 V. If inductance, $L = 20\ \text{mH}$, resistance, $R = 80\ \Omega$, and capacitance, $C = 400\ \text{nF}$, determine (a) the resonant frequency, (b) the value of the p.d. across the capacitor at the resonant frequency, (c) the frequency at which the p.d. across the capacitor is a maximum, and (d) the value of the maximum voltage across the capacitor.

13 K2 CO3

(OR)

- b) A pure inductance of $150\ \text{mH}$ is connected in parallel with a $40\ \mu\text{F}$ capacitor across a $50\ \text{V}$, variable frequency supply. Determine
- Resonant frequency of the circuit
 - Current circulating in the capacitor and inductance at resonance

7 K2 CO3

6

14. a) A $415\ \text{V}$, 3-phase ac motor has a power output of $12.75\ \text{KW}$ and operates at a power factor of 0.77 lagging with an efficiency of 85% . If the motor is delta-connected, Determine

- Power input
- Line current and phase current

5 K2 CO4

8


(OR)

- b) A balanced star-connected load absorbs a total power of $5\ \text{KW}$ at a leading power factor of 0.6 when connected to a line voltage of $240\ \text{V}$. Find the impedance of each phase and total complex power of load.

13 K1 CO4

15. a) Obtain 'Y' – parameters for the given network shown in below figure.


13 K2 CO5

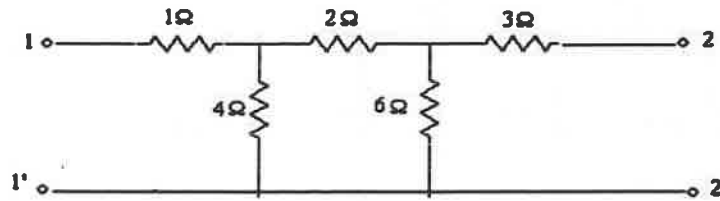

(OR)

b) Determine the h parameters for the circuit shown in below figure.

13 K2 CO5

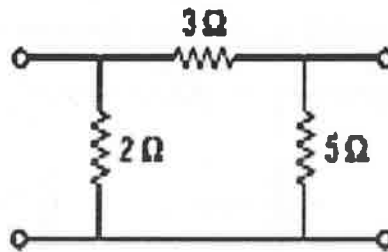

PART – C

(1 x 15 = 15 Marks)

Q.No.	Questions	Marks	KL	CO
16. a)	Derive the expression for the voltage across the inductor and capacitor in a series RLC circuit ($R = 5\Omega$, $L = 5\text{mH}$, $C = 5\mu\text{F}$) excited by a sinusoidal voltage of 100V, 50 Hz if the supply is connected at $t = 0$. Assume zero initial conditions.	15	K3	CO5
	(OR)			
b)	A parallel RL circuit is connected to an A.C voltage $v = 100\sin(500t+300)$ at $t = 0$. If $R = 5$ ohms and $L = 0.01\text{H}$, find the equation for the current.	15	K3	CO5